

# Synchronous Machine Tests and Synchronization

Soham Karanjikar (Recorder)

Partners: Luis Aragon (Leader)

Performed: March 5th 2020

Written: March 24th 2020

## I INTRODUCTION

The objective of this lab was to get exposed to synchronous motors and see how to work with them. We did a few tests first to get parameters of the motor then proceeded to synchronize it with the grid using the light bulb method. This lab was quick and not tedious to complete, however still gave a good understanding of synchronous motors.

*All data/measurements taken are provided in the appendix at the bottom of the document.*

## 2 RESULTS

### 2.1 Open/Short Circuit Tests

The first part of this lab was to characterize the motor. We completed tests similar to the induction motor lab to get parameters of this motor.


**Table 1: Open Circuit Data**

Rf2 (Ohms)	Field Current (A)	Armature Current (A)	Va (V)
infinity	0	0	.82
500	.308	0	44.9
250	.530	0	75.6
166	.689	0	96.3
125	.814	0	111.4
100	.917	0	122.4
83.3	.988	0	129.4
71.43	1.05	0	134.9
62.5	1.10	0	138.9
55.56	1.15	0	142.04
50	1.20	0	144.6


**Table 2: Short Circuit Data**

Rf2 (Ohms)	Field Current (A)	Armature Current (A)	Va (V)
infinity	0	.318	.13
500	.308	2.37	4.02
250	.529	4.07	6.99

*Fig.1 OCC and SCC Data*

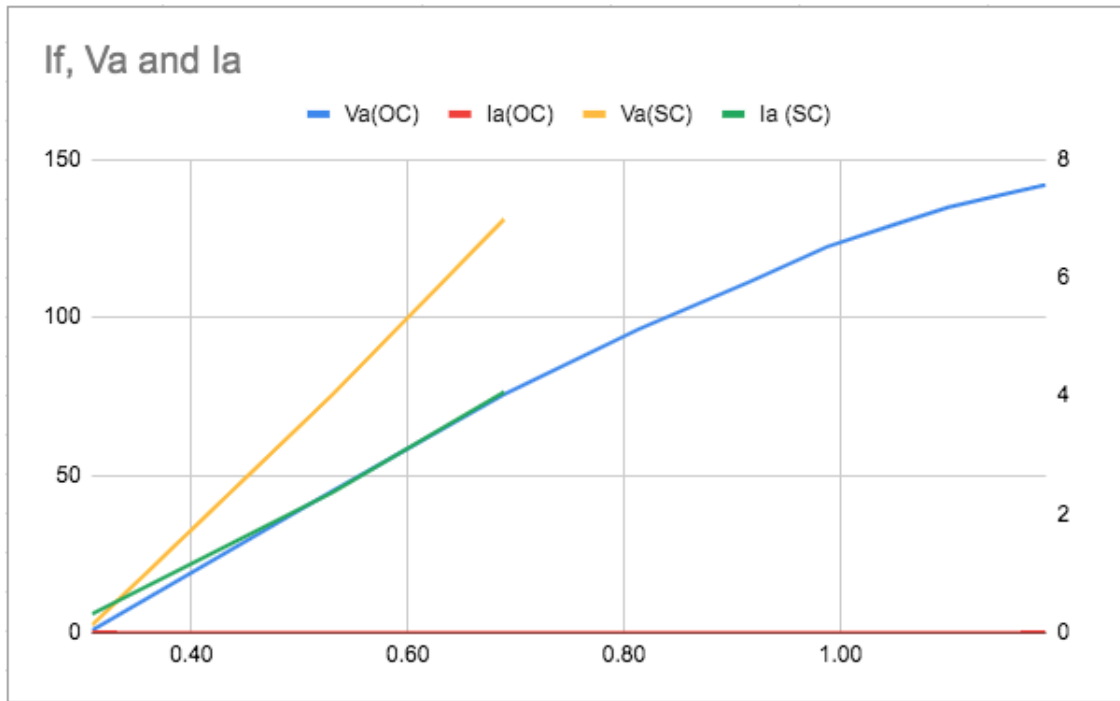

*Fig.2 OCC and SCC Data (only Ia SC and Va OC)*

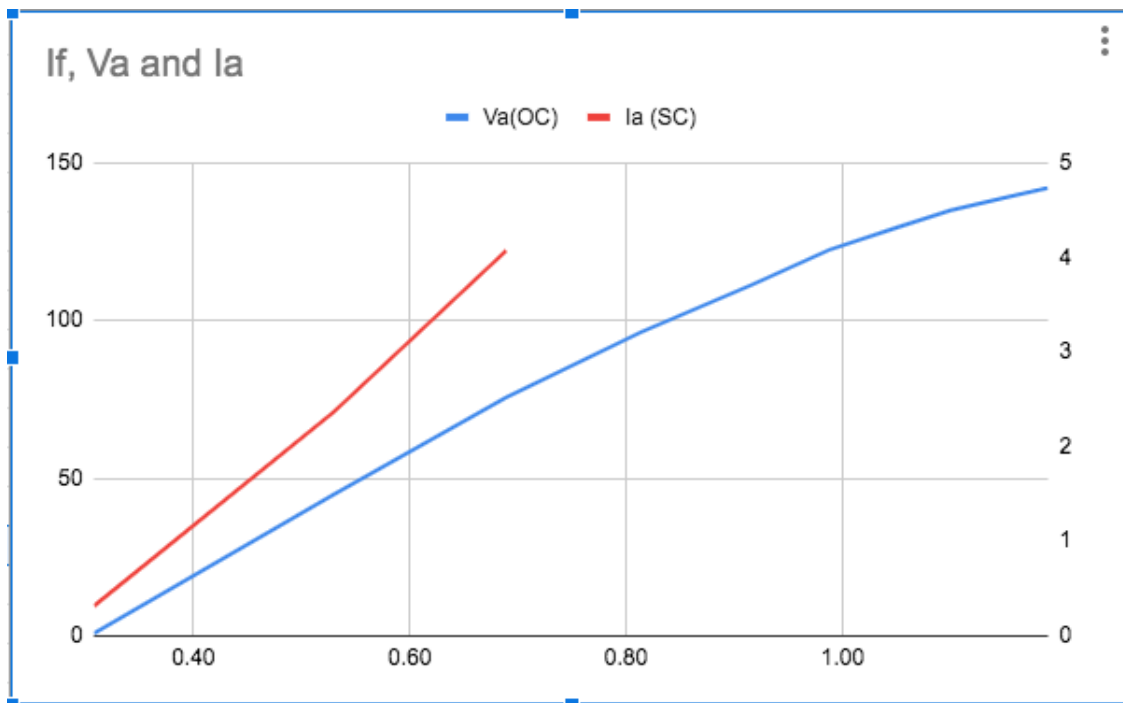

With this data we can calculate  $K_f$  and  $x_s$  (saturated and unsaturated).

$$E_a = K_f \cdot \omega \cdot I_f$$

Equation 1.

It is evident that  $K_f$  is just the slope of  $V_a$  vs  $I_f$ .

Thus the **unsaturated  $K_f = 138.58$**  and **saturated  $K_f = 51.2$**

Similarly we can calculate  $x_s$  with the following equation:

$$x_s = \frac{V_a}{I_a} \quad \text{Equation 2.}$$


So **unsaturated  $x_s = 0.409$  ohms** and **saturated  $x_s = 1.72$  ohms**

## 2.2 Motor Synchronization

In this part of the lab we used lights to synchronize the motor to the wall outlets. We did so by adding the lights between the 3 phases of our power supply and 3 phases of the motor. When the lights were completely off it shows that the voltage difference between the two sides is 0 and the motor is synchronized with the supply. We adjusted the motor's speed using **Torque modulation** and once the lights were cycling on and off slowly we knew we had the right timing. We were basically adjusting  $I_f$  to change motor speed until it was easy for us to see synchronization.


## 2.3 Experimental Diagram

Fig.3 Unsaturated Circuit Diagram

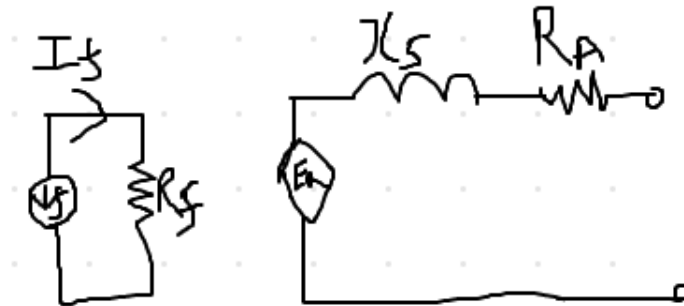

$$R_f = 128.3, X_s = 0.409, R_A = 0.72$$

Fig.4 Saturated Circuit Diagram

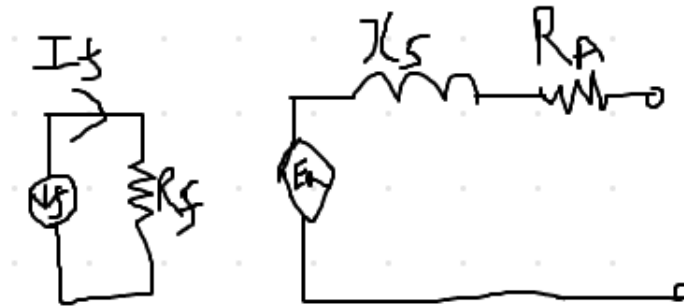

$$R_f = 128.3, X_s = 1.72, R_A = .72$$

### 3 CONCLUSION

This lab gave us a good look into synchronous machines and how they are operated to work like we want. The experiments we did showed the benefits of using synchronous motors and how they are more efficient. Further we also inspected torque vs current effect and how higher rotor resistance affected Voltage and field current. The OCC and SCC allowed us to get values to draw the equivalent circuit, similar to an induction motor.

### 4 REFERENCES

[1] P.W. Sauer, P.T. Krein, P.L. Chapman, *ECE 431 Electric Machinery Course Guide and Laboratory Information*, University of Illinois at Urbana-Champaign, 2005.

## 5 APPENDIX

Raw Data:

50

Lab 6

Diode A

Field Resistance = 12.9.3.51

Armature Resistance = 7.2.2

Rf 2	Field Current	Armature current	V <sub>A</sub> -V <sub>f</sub> (mV)
∞	0.125 A	0	8.2
500	0.309 A	0	44.4
250	0.550 A	0	75.6
166	0.689 A	0	96.3
125	0.814	0	111.4
100	0.918	0	122.4
83.3	0.988	0	129.4
71.43	1.05	0	134.9
62.5	1.10	0	138.9
55.56	1.15	0	142.04
50	1.19	0	144.6
Scattered Results			
Open	0	3.8	-13V
500	0.305	2.37	4.02
250	0.509	1.107	6.49
125			
Diode C			
Turned			
17.0	Power	V <sub>avg</sub> (V <sub>avg</sub> )	I <sub>f</sub>
14.6	-2.2W	1.20.22V	0.85
	50	1.20.23	0.85
			1.7
			1.7

R<sub>f</sub> is not  
corrected