

ECE 431 Homework #4 (Due – Wednesday March 04 2020)

Problem 4.1

The single-phase equivalent-circuit parameters for a three-phase induction motor in ohms-per-phase are

$$R_1=0.2 \, \Omega, R_2'=0.24 \, \Omega, X_1=1, X_2=0.8, \, \Omega, X_m=80 \, \Omega, R_c=300 \, \Omega$$

For a slip of 3.5 percent, and a terminal voltage of 460 V, line-line, calculate:

- The motor phase current and input real and reactive power
- The mechanical output power and the power dissipated in the rotor. You may assume that the motor friction and windage losses are 300 W
- The motor core loss and the motor efficiency

Problem 4.2

You have been asked to assess the suitability of an induction motor with the following parameters:

3-phase, 480V, 60Hz, 1170 rpm,

$$R_1=0.5 \, \Omega, R_2'=0.5 \, \Omega, X_1=X_2'=1 \, \Omega, X_m=100 \, \Omega, R_c=300 \, \Omega$$

The motor is required to drive a load given by $T_{load} = 150 + 0.5 \, \omega_m$ Nm.

Use Thevenin equivalent and neglect mechanical losses in the motor.

- Will the motor start?
- What is the starting current?
- At what speed and slip will it run?
- What is the efficiency?
- At what power factor will it operate?